

Loops and Orbits - Homework 3 - Capacitor

the equation

$$V_0 = IR + \frac{Q}{C}$$

Annotations:
- V_0 : DC supply
- I : current
- R : resistance
- Q : charge
- C : capacitance

DUE FRIDAY
1/24, BY END
OF OFFICE
HOURS

was turned into a model the computer can handle as follows:

$$V_0 = \frac{Q_{i+1} - Q_i}{t_{i+1} - t_i} R + \frac{Q_i}{C}$$

Rearrange

$$Q_{i+1} = Q_i + \frac{t_{i+1} - t_i}{R} \left(V_0 - \frac{Q_i}{C} \right)$$

So that tells you how to get charge-after from charge-before

This is an easy model but a hard homework because for the first time I want you to produce the notebook on your own. You are welcome to borrow code from any of our other notebooks.

At the end of your notebook should be a graph of $\frac{Q}{C}$ as a function of time

Turn in that graph by 2pm on Friday as your completed homework.